

2 *A Simple Logic Gate*


- This experiment introduces the student to a simple logic element, an **inverter**, contained in a 14 Dual-in-line (DIP) package. The student will use equipment skills learned in the first lab to measure the **propagation delay** of the inverter.

I. 7404 Logic Gate

Appendix I contains the datasheet for a 7404 logic gate. Datasheets for 74XX family devices can be found on the WWW at the Texas Instruments data sheet web site:

<http://www.ti.com/sc/docs/products/logic/index.htm>

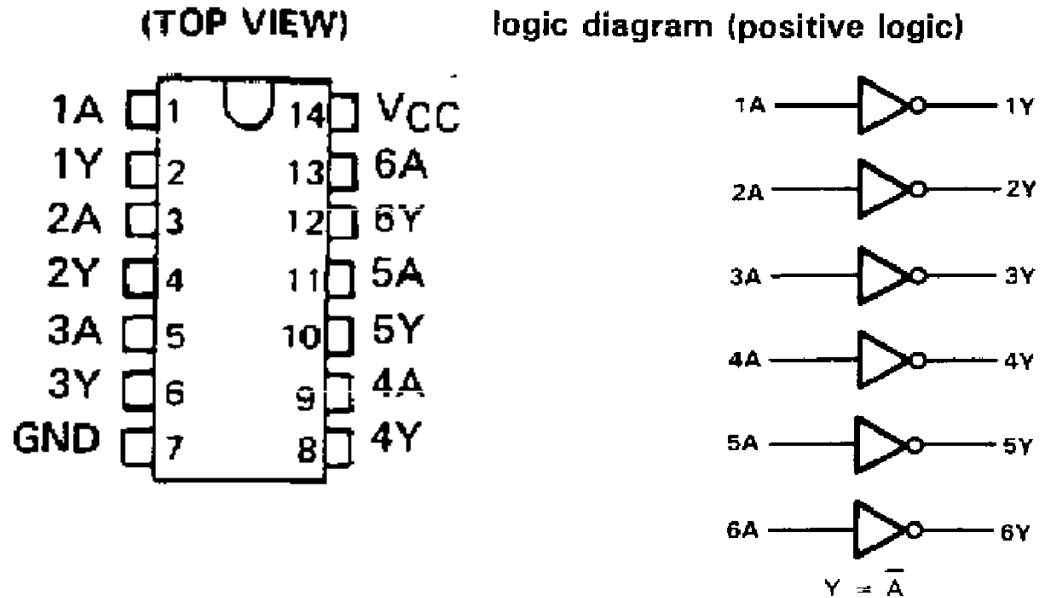Datasheets can also be found in your TTL logic databook. Below is the pinout for the 7404 (in future labs, you will be expected to look up the datasheet yourself on the WWW or in your databook and have the datasheets with you in lab).



The VCC pin should be connected to +5 V for this part, GND is connected to the COM terminal on the test box. Note that pin #1 is to the left of the “notch” located at one end of IC; the notch is used to locate pin #1.

- A. With the testbox OFF, connect a 7404 IC chip as follows.
1. +5V to pin #14
 2. GND to pin #7
 3. Data Switch 1 (DS-1) to pin #1
 4. Data Indicator 1 (DI-1) to pin #2
- B. After your instructor checks your circuit, turn the breadboard on.
- C. Observe the LED output and measure both the input and the output voltages using the digital multimeter with the data switch in both positions (record measurements on datasheet at end of lab). Repeat these measurements after connecting in parallel the five remaining inverters to the output of the first (this checks to see if one inverter output can drive the inputs of 5 inverters simultaneously).

II. Lab Data Sheet

(A)
Single logic **INVERTER**

TA CHECK OFF SIGNATURE: _____

| | Input (V) | Logic Input | Output (V) | Logic Output |
|--------|-----------|-------------|------------|--------------|
| “Up” | | | | |
| “Down” | | | | |

One **INVERTER** driving 5 inverters:

| | Input (V) | Logic Input | Output (V) | Logic Output |
|--------|-----------|-------------|------------|--------------|
| “Up” | | | | |
| “Down” | | | | |

(F) Six Inverters, Sketch the input and output waveforms (Label TPHL, TPLH propagation delays on sketch!!)

Measured TPHL propagation delay thru 6 inverters: _____ Average Delay: _____

Measured TPLH propagation delay thru 6 inverters: _____ Average Delay: _____

(G) Five INVERTERS

Measured TPHL propagation delay thru 5 inverters: _____ Average Delay: _____

Measured TPLH propagation delay thru 5 inverters: _____ Average Delay: _____

LOCATE the propagation delay given in the DATA SHEET for the 7404 and COMPARE THIS VALUE to the values above.

Comments on 7404 data sheet propagation delay and measured average delay:

Formulas:

$$\text{Propagation delay, } t_{pxx} = \frac{\Delta t}{M * G} \text{ seconds}$$

Δt = Time difference between CH1 and CH2.

M = multiplier used on the oscilloscope (will usually be 1 or 10)

G = number of logic gates used.

$$\text{Frequency} = \frac{1}{\text{Period}}$$


Appendix I: Propagation Delay

Propagation delay is the delay from a change on an input to a change on the output.

TPHL is the propagation delay for an input change causing a HIGH to LOW change on the output (this does NOT REFER to input change). TPLH is the propagation delay for an input change causing a LOW to HIGH change on the output.

The figures below define TPHL, TPLH for inverting and non-inverting gates.

Propagation Delay (inverting)

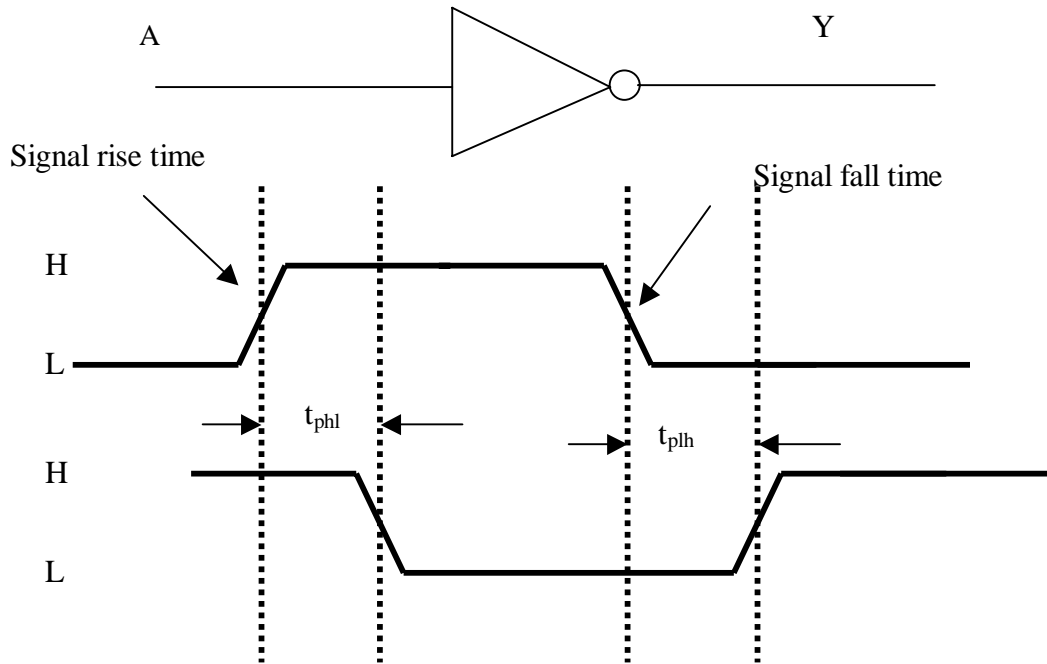

Propagation Delay (non inverting)

