 



Homebrewing RISCs in FPGAs

Jan Gray (jsgray@acm.org)



lbu r1, 4(r31)


Introduction

 

lbu r1, 4(r31)

- ▼ Recent dense programmable logic enables affordable “desktop processor development”
- ▼ Example: J32: 32-bit RISC at 16 MIPS (1995)
 - ▼ classic 32-bit RISC
 - ▼ 32 registers, 3-operand architecture
 - ▼ classic μ arch: 4-stage pipeline (IF/RF/EX/WB)
 - ▼ on-chip peripherals
 - ▼ 32-bit bus, boot ROM, UART, DRAM control, ...


Talk Outline

 

lbu r1, 4(r31)

- ▼ FPGAs
- ▼ Xilinx XC4000 architecture
- ▼ Design Process, CNets HDL
- ▼ J32: architecture, μ arch, floorplan, peripherals
- ▼ Demo
- ▼ Ongoing work
- ▼ References, Resources

Field Programmable Gate Arrays

 


- ▼ Evolved from PALs, PLDs, Complex PLDs
- ▼ A niche hardware implementation technology

Technology	Gates	Speed	NRE Cost	Part Cost	Spin time
Custom VLSI	<10M	<500 MHz	\$20K-\$100M	\$1-up	weeks
Gate array	<2M	<200 MHz	\$10K-\$1M	\$1-up	days/weeks
FPGA	<100K	<100 MHz	\$100-\$100K	\$10-\$1K	minutes/hours

- ▼ Strengths: quick prototyping and time-to-market, reprogrammability, relatively easy to use
- ▼ Weaknesses: cost, density, speed
- ▼ Vendors: Xilinx, Altera, Actel, Atmel, Lucent, Cypress, QuickLogic, IBM, Motorola


FPGA Technologies

 

lbu r1, 4(r31)

- ▼ Programmable Elements
 - ▼ Logic blocks
 - ▼ combinatorial: lookup tables (LUTs) or gates + muxes
 - ▼ sequential: flip-flops
 - ▼ Interconnect: metal wire segments connected by...
 - ▼ pass transistors driven by SRAM or EEPROM bit cells
 - ▼ fuses or antifuses (one-time programmable)
- ▼ FPGA architecture variations
 - ▼ CLB arrays, rows, macrocells; fine/coarse grain
 - ▼ RAM, fast wide adders, TBUFs (3-state buffers)


FPGAs: Easy to Use

 

lbu r1, 4(r31)

- ▼ Idealized digital design model
 - ▼ No analog EE: ignore gate and wire capacitances, transistor W/L ratios, etc.
 - ▼ Low skew global nets \Rightarrow No clock skew worries
 - ▼ Buffered line drivers \Rightarrow No gate fan-out worries
- ▼ Synchronous design “just works”
 - ▼ Avoid async. flip-flop state changes, gated clocks
 - ▼ Try to keep everything on one device
 - ▼ Design, simulate, it *should* just work
 - ▼ ...even if you’re just a software type
- ▼ But, effort to master effective use of resources


FPGA Applications

 

lbu r1, 4(r31)

- ▼ Conventional: cheap, fast turnaround, field upgradable ASICs (J32)
- ▼ Some reconfigurable applications
 - ▼ Quickturn: fast design simulation/verification
 - ▼ Signal, image processing: filters, warping, music
 - ▼ Graphics: span and octree rendering acceleration
 - ▼ Military: target dependent correlation/recognition
 - ▼ Cryptography: DES search
 - ▼ “Hardware” genetic algorithms


Xilinx XC4000 FPGA

 

lbu r1, 4(r31)

- ▼ Introduced in 1992, Xilinx's third generation
- ▼ Device family spans 3,000 to 125,000 "gates", 2 ns to 6 ns gate delays, \$20 to \$1000 Q1
- ▼ J32 uses XC4010PC84-5
 - ▼ 20x20 Configurable Logic Blocks, 60 I/Os, 5 ns gate delay, \$150


XC4000

 

Configurable Logic Block

- ▼ Two 4-input LUTs and one 3-input LUT
 - ▼ Two $f(a,b,c,d)$, or $f(a,b,c,d,e, \dots)$, 5 or 7 ns delay
- ▼ Two flip-flops w/ clock enable, reset/set
 - ▼ 0 ns setup if input is its LUT
- ▼ Special features:
 - ▼ Writeable LUTs provide 32x1 or 16x2 SRAM
 - ▼ 32 CLBs make a 32x32 register file
 - ▼ Dedicated fast ripple carry chain hardware
 - ▼ 16 CLBs implement 32-bit adder, ~35 ns delay
- ▼ *Fig. 1*


XC4000 Interconnect

 

Ibu r1, 4(r31)

- ▼ Hierarchical resources for hierarchical circuits
 - ▼ More/better connections to neighbouring CLBs
- ▼ Wires per CLB:
 - ▼ 8 horizontal + 8 vertical local interconnect
 - ▼ 4H+4V double-length: connect every other CLB
 - ▼ 6H+6V long lines (2H w/ TBUFs): connect CLBs on a row or column: *buses and control lines*
 - ▼ 4V global: *low-skew clock drivers*
 - ▼ 2V carry-chain: *fast wide adders/comparators*
- ▼ *Fig. 29, 26, 27*


XC4000 I/O Block

 

Ibu r1, 4(r31)

- ▼ Input: direct, registered
- ▼ Output: direct, registered, 3-stated, pull-ups/pull-downs, slew rate options
- ▼ Some IOB pads not bonded to package pins
- ▼ *Fig. 16*


FPGA Development Process

 

l bu r1, 4(r31)

- ▼ Design capture: schematics, custom tools, hardware design languages; *must floorplan!*
- ▼ Simulate/Verify: *oh well*
- ▼ Compile: “technology mapping”, place, route
- ▼ Make config bitstream: XC4010: 178,000 bits
- ▼ Download:
 - ▼ “master load” from byte-wide or bit-serial ROM
 - ▼ “slave load” by microprocessor or XChecker pod
- ▼ Test/Debug: pod can readback internal state!


CNets HDL

 

lbu r1, 4(r31)

- ▼ C++ class library for Xilinx FPGAs
 - ▼ Nets, buses, gates, primitives, modules
 - ▼ Intuitive notation courtesy overloaded operators
 - ▼ C++-based design is compiled, run, emits XNF
- ▼ Motivation
 - ▼ Inadequacies and costs of schematic capture, Verilog/VHDL synthesis and simulation
 - ▼ Power of general purpose programming language
 - ▼ Explicit control
 - ▼ Placement constraints to achieve floor plan
 - ▼ Map particular gate expressions into CLBs

J32 Instruction Set

 

lbu r1, 4(r31)

▼ Instructions

- ▼ add/sub, and/or/xor/xnor, shift/rotate left/right 1,2,4
- ▼ load/store byte/half/word signed/unsigned
- ▼ jump conditional, jump-and-link (two delay slots)


▼ Condition codes: Zero, Neg, Carry, oVerflow

- ▼ ZNCV on add/sub, ZN.. on op/ld, no change on st/j

▼ Formats

- ▼ op reg: { 0|op:4|0 rd:5 ra:5 rb:5 } : add r3,r1,r2
- ▼ op imm: { 0|op:4|1 rd:5 ra:5 im:16 } : add r3,r1,42
- ▼ ld/st/j: { 1|op:5 rd:5 ra:5 im:16 } : lbu r1,42(r31)


J32 Design Process

 

lbu r1, 4(r31)


- ▼ Evolve “unrealized” 16-bit microcode design
- ▼ DLX-like ISA to run C code; DLX-like μ arch
- ▼ Architecture/microarchitecture codesign
 - ▼ Try mapping structures into FPGA elements
 - ▼ Iterative floorplanning
 - ▼ Example: ld/st byte/halfword requires byte-lane alignment hardware; feasible using TBUFs!

Missing/Compromised Features

 

- ▼ No barrel shifter: 1-, 2-bit shifts only
- ▼ Jumps
 - ▼ Reuse effective address adder
 - ▼ Saves adder, multiplexor, much interconnect
 - ▼ No PC-relative “branch” instructions
 - ▼ 2 cycle branch delay
 - ▼ Two branch delay slots
 - ▼ Better to annul some, give 0, 1, 2 delay slot versions?
- ▼ 1+ cycle load/store pipe *stall*
 - ▼ Share one memory port


J32 Design Process (2)

 

lbu r1, 4(r31)

- ▼ Challenge: minimize interconnect needs
 - ▼ Multiplex any result onto shared 32-bit bus
 - ▼ Adder, logic, shifts, load, sign-extensions, store, PC
- ▼ Critical paths
 - ▼ Register file: result writeback and operand read
 - ▼ Execute: operand register, adder, result mux, bypass mux, operand register
 - ▼ Memory (lbs): address out, address decode, memory access, result byte alignment, sign ext., result mux, bypass mux, operand register


J32 Pipeline Stages

 

lbu r1, 4(r31)

- ▼ IF: Instruction Fetch
 - ▼ MAR out; incr. PC; access mem; latch instruction
- ▼ RF: Decode and Register File access
 - ▼ Decode instruction; read register operands; sign ext. immediate field; select operands
- ▼ EX: Execute
 - ▼ Add/effective address; logic; shift; select result
 - ▼ j: load MAR, PC with ea
 - ▼ ld/st: load MAR with ea, stop pipe for mem access
- ▼ WB: Write Back results to register file

J32 Pipeline Hazards

 

l bu r1, 4(r31)

- ▼ Problem: result dependencies

```
add r1, r1, 1   IF RF EX WB
ld  r2, 0(r1)   IF RF EX WB
```

- ▼ Fix: Software: reorder instructions/insert nops

- ▼ Fix: Stall pipeline (not used)



```
add r1, r1, 1   IF RF EX WB
ld  r2, 0(r1)   IF -- RF EX WB
```

- ▼ Fix: register forwarding (register file bypass)


```
add r1, r1, 1   IF RF EX WB
ld  r2, 0(r1)   IF RF EX WB
```

- ▼ Compromise: A operand only


J32 Microarchitecture

  


J32 Floorplan

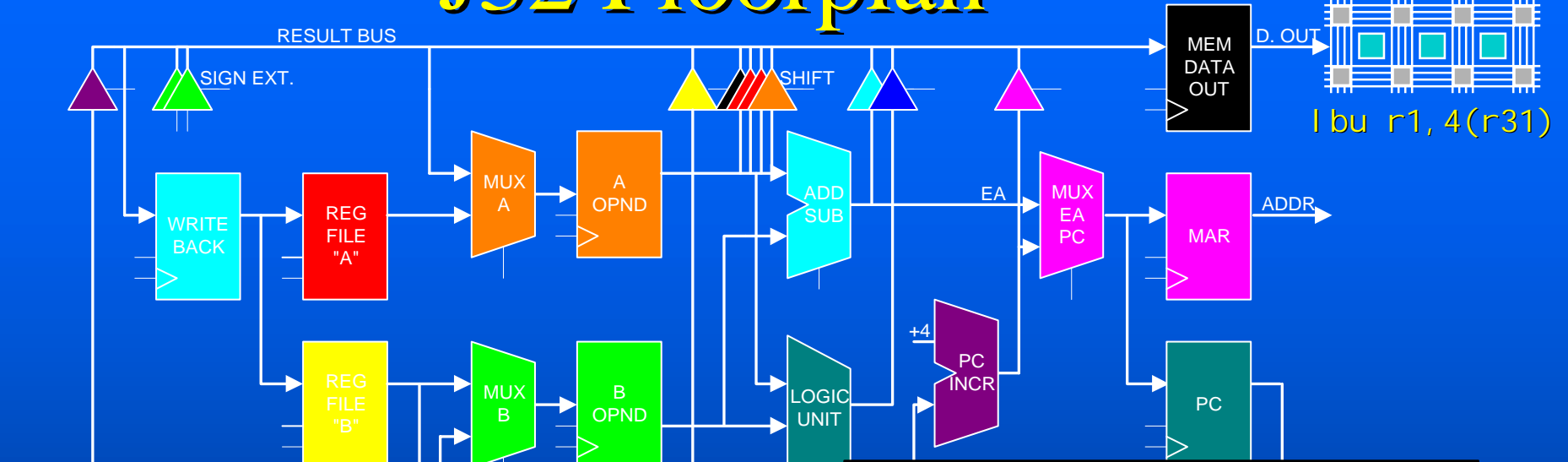

`l bu r1, 4(r31)`

 


J32 Control Unit

 

lbu r1, 4(r31)

- ▼ Hardwired control
- ▼ Sequence clock phases


J32 Integrated Peripherals

 

l bu r1, 4(r31)

- ▼ 32-bit on-chip memory/peripherals bus
 - ▼ Address decoding, ack, wait-state insertion
 - ▼ Subwords: byte enables, byte-lane shifters
- ▼ 32-word boot “ROM”
- ▼ UA(R)T
 - ▼ Baud rate generator, shift register, busy arbiter
- ▼ (DRAM controller)
 - ▼ State machine, address mux, RAS/ CAS/, refresh
 - ▼ Fast page mode: page address register, comparator


Future Plans

 

lbu r1, 4(r31)

- ▼ Redesign CNets as Java HDL, add simulator
- ▼ Retarget XC4000E
- ▼ Interpreter, operating system
- ▼ “J64”
- ▼ 3D rendering accelerator

References

 

lbu r1, 4(r31)


▼ FPGAs

- ▼ Xilinx, The Programmable Logic Data Book, 1994
- ▼ Trimberger, S., Field-Programmable Gate Array Technology, Kluwer.

▼ RISC architecture/implementation

- ▼ Hennessey and Patterson, Computer Architecture: A Quantitative Approach, also ... Morgan Kaufman
- ▼ Fielding, Computer Architecture, A Designer's Text Based on a Generic RISC, ...

Resources

 

lbu r1,4(r31)

- ▼ Usenet: [comp.arch.fpga](#), [comp.arch](#)
- ▼ Web
 - ▼ [www.xilinx.com](#), [www.altera.com](#), ...
 - ▼ [www.io.com/~guccione/HW_list.html](#)
 - ▼ [www.mrc.uidaho.edu/fpga/fpga.html](#),
[www.super.org:8000/FPGA](#)
- ▼ Conferences
 - ▼ SIGDA Int'l Symp. on FPGAs, Monterey, Feb.
 - ▼ IEEE Symp. on FPGAs for Custom Computing Machines, Napa, April