



Digital Design

Chapter 5: Register-Transfer Level (RTL) Design

Slides to accompany the textbook *Digital Design*, First Edition,
by Frank Vahid, John Wiley and Sons Publishers, 2007.
<http://www.ddvahid.com>




Copyright © 2007 Frank Vahid

Instructors of courses requiring Vahid's Digital Design textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as unanimated pdf versions on publicly-accessible course websites. PowerPoint source (or pdf with animations) may not be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley – see <http://www.ddvahid.com> for information.

   5.1

Introduction

- Chapter 3: Controllers
 - Control input/output: single bit (or just a few) representing event or state
 - Finite-state machine describes behavior; implemented as state register and combinational logic
- Chapter 4: Datapath components
 - Data input/output: Multiple bits collectively representing single entity
 - Datapath components included registers, adders, ALU, comparators, register files, etc.
- This chapter: custom **processors**
 - Processor: Controller and datapath components working together to implement an algorithm




Digital Design
Copyright © 2006
Frank Vahid

Note: Slides with animation are denoted with a small red "a" near the animated items

2

RTL Design: Capture Behavior, Convert to Circuit

- Recall
 - Chapter 2: Combinational Logic Design
 - First step: Capture behavior (using equation or truth table)
 - Remaining steps: Convert to circuit
 - Chapter 3: Sequential Logic Design
 - First step: Capture behavior (using FSM)
 - Remaining steps: Convert to circuit
- RTL Design (the method for creating custom processors)
 - First step: Capture behavior (using high-level state machine, to be introduced)
 - Remaining steps: Convert to circuit

 


RTL Design Method

Step	Description
Step 1 <i>Capture a high-level state machine</i>	Describe the system's desired behavior as a high-level state machine. The state machine consists of states and transitions. The state machine is "high-level" because the transition conditions and the state actions are more than just Boolean operations on bit inputs and outputs.
Step 2 <i>Create a datapath</i>	Create a datapath to carry out the data operations of the high-level state machine.
Step 3 <i>Connect the datapath to a controller</i>	Connect the datapath to a controller block. Connect external Boolean inputs and outputs to the controller block.
Step 4 <i>Derive the controller's FSM</i>	Convert the high-level state machine to a finite-state machine (FSM) for the controller, by replacing data operations with setting and reading of control signals to and from the datapath.



RTL Design Method: "Preview" Example

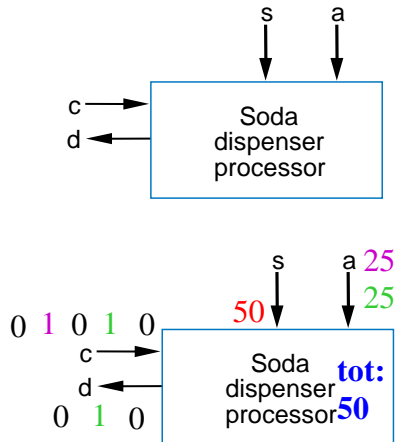- Soda dispenser
 - c : bit input, 1 when coin deposited
 - a : 8-bit input having value of deposited coin
 - s : 8-bit input having cost of a soda
 - d : bit output, processor sets to 1 when total value of deposited coins equals or exceeds cost of a soda



How can we precisely describe this processor's behavior?




Digital Design
Copyright © 2006
Frank Vahid

5

Preview Example: Step 1 -- Capture High-Level State Machine

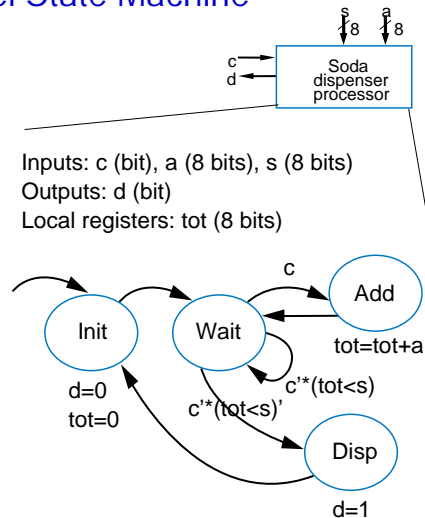- Declare local register tot
- **Init** state: Set $d=0$, $tot=0$
- **Wait** state: wait for coin
 - If see coin, go to **Add** state
- **Add** state: Update total value: $tot = tot + a$
 - Remember, a is present coin's value
 - Go back to **Wait** state
- In **Wait** state, if $tot \geq s$, go to **Disp**(ense) state
- **Disp** state: Set $d=1$ (dispense soda)
 - Return to **Init** state




Digital Design
Copyright © 2006
Frank Vahid

6

Preview Example: Step 2 -- Create Datapath

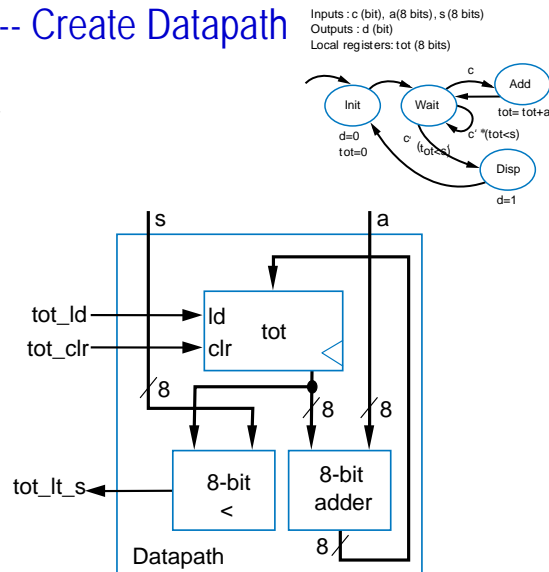- Need *tot* register
- Need 8-bit comparator to compare *s* and *tot*
- Need 8-bit adder to perform $tot = tot + a$
- Wire the components as needed for above
- Create control input/outputs, give them names




Digital Design
Copyright © 2006
Frank Vahid

7

Preview Example: Step 3 – Connect Datapath to a Controller

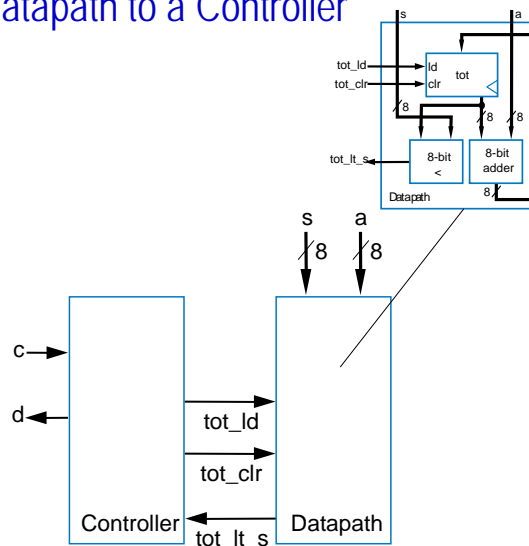- Controller's inputs
 - External input *c* (coin detected)
 - Input from datapath comparator's output, which we named *tot_lt_s*
- Controller's outputs
 - External output *d* (dispense soda)
 - Outputs to datapath to load and clear the *tot* register




Digital Design
Copyright © 2006
Frank Vahid

8

Preview Example: Step 4 – Derive the Controller's FSM

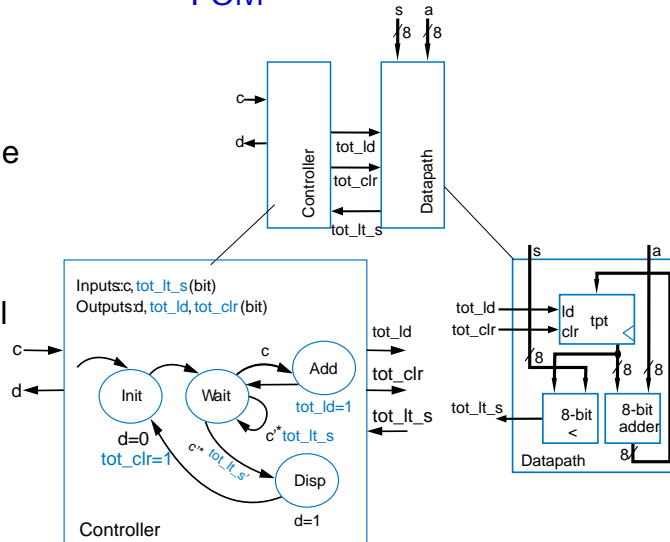- Same states and arcs as high-level state machine
- But set/read datapath control signals for all datapath operations and conditions




Digital Design
Copyright © 2006
Frank Vahid

9

Preview Example: Completing the Design

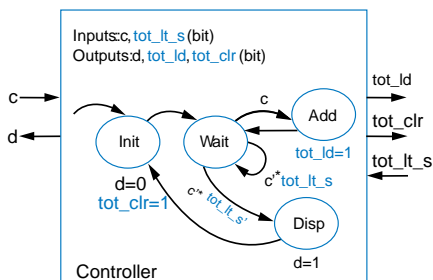- Implement the FSM as a state register and logic
 - As in Ch3
 - Table shown on right



	s1	s0	c	tot_ld_s	n1	n0	d	tot_ld	tot_clr
Init	0	0	0	0	0	1	0	0	1
	0	0	0	1	0	1	0	0	1
	0	0	1	0	0	1	0	0	1
	0	0	1	1	0	1	0	0	1
Wait	0	1	0	0	1	1	0	0	0
	0	1	0	1	0	1	0	0	0
	0	1	1	0	1	0	0	0	0
	0	1	1	1	1	0	0	0	0
Add	1	0	0	0	0	1	0	1	0

Disp	1	1	0	0	0	0	1	0	0




Digital Design
Copyright © 2006
Frank Vahid

10

Step 1: Create a High-Level State Machine

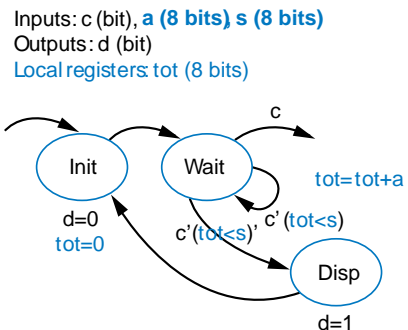
- Let's consider each step of the RTL design process in more detail
- Step 1
 - Soda dispenser example
 - Not an FSM because:
 - Multi-bit (data) inputs a and s
 - Local register tot
 - Data operations $tot=0$, $tot < s$, $tot=tot+a$.
 - Useful high-level state machine:
 - Data types beyond just bits
 - Local registers
 - Arithmetic equations/expressions



Digital Design
 Copyright © 2006
 Frank Vahid

11

 Step 1 Example: Laser-Based Distance Measurer




- Example of how to create a high-level state machine to describe desired processor behavior
- Laser-based distance measurement – pulse laser, measure time T to sense reflection
 - Laser light travels at speed of light, $3 \cdot 10^8$ m/sec
 - Distance is thus $D = T \text{ sec} * 3 \cdot 10^8 \text{ m/sec} / 2$



Digital Design
 Copyright © 2006
 Frank Vahid

12

 Step 1 Example: Laser-Based Distance Measurer



- Inputs/outputs

- B : bit input, from button to begin measurement
- L : bit output, activates laser
- S : bit input, senses laser reflection
- D : 16-bit output, displays computed distance




Digital Design
Copyright © 2006
Frank Vahid


13

Step 1 Example: Laser-Based Distance Measurer

 Inputs: B , S (1 bit each)
Outputs: L (bit), D (16 bits)



 $L = 0$ (laser off)
 $D = 0$ (distance = 0)



- Step 1: Create high-level state machine
- Begin by declaring inputs and outputs
- Create initial state, name it **S0**
 - Initialize laser to off ($L=0$)
 - Initialize displayed distance to 0 ($D=0$)





Digital Design
Copyright © 2006
Frank Vahid

14

Step 1 Example: Laser-Based Distance Measurer

  Inputs: B, S (1 bit each)
Outputs: L (bit), D (16 bits)



- Add another state, call **S1**, that waits for a button press
 - B' – stay in **S1**, keep waiting
 - B – go to a new state **S2**

Q: What should S2 do? A: Turn on the laser





Digital Design
Copyright © 2006
Frank Vahid

15

Step 1 Example: Laser-Based Distance Measurer

  Inputs: B, S (1 bit each)
Outputs: L (bit), D (16 bits)



- Add a state **S2** that turns on the laser (L=1)
- Then turn off laser (L=0) in a state **S3**

Q: What do next? A: Start timer, wait to sense reflection




Digital Design
Copyright © 2006
Frank Vahid

16

Step 1 Example: Laser-Based Distance Measurer

Inputs: B, S (1 bit each) Outputs: L (bit), D (16 bits)

Local Registers: Dctr (16 bits)

 

- Stay in **S3** until sense reflection (S)
- To measure time, count cycles for which we are in **S3**
 - To count, declare local register *Dctr*
 - Increment *Dctr* each cycle in **S3**
 - Initialize *Dctr* to 0 in **S1**. **S2** would have been O.K. too




Digital Design
Copyright © 2006
Frank Vahid

17

Step 1 Example: Laser-Based Distance Measurer

Inputs: B, S (1 bit each) Outputs: L (bit), D (16 bits)

Local Registers: Dctr (16 bits)

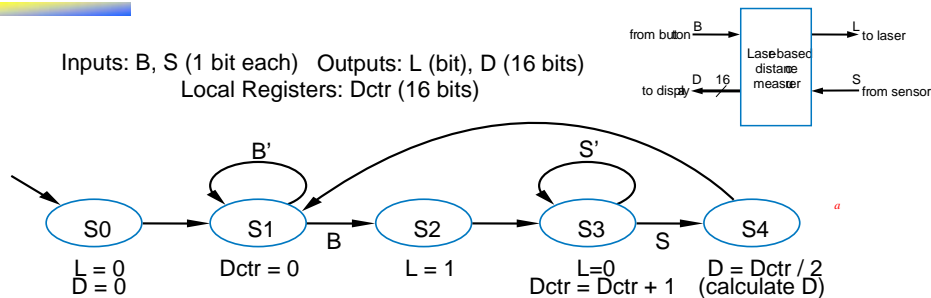

- Once reflection detected (S), go to new state **S4**
 - Calculate distance
 - Assuming clock frequency is 3×10^8 , *Dctr* holds number of meters, so $D = Dctr / 2$
- After **S4**, go back to **S1** to wait for button again



Digital Design
Copyright © 2006
Frank Vahid

18

Step 2: Create a Datapath


- Datapath must
 - Implement data storage
 - Implement data computations
- Look at high-level state machine, do three substeps
 - (a) Make data inputs/outputs be datapath inputs/outputs
 - (b) Instantiate declared registers into the datapath (also instantiate a register for each data output)
 - (c) Examine every state and transition, and instantiate datapath components and connections to implement any data computations

Instantiate: to introduce a new component into a design.




Step 2 Example: Laser-Based Distance Measurer

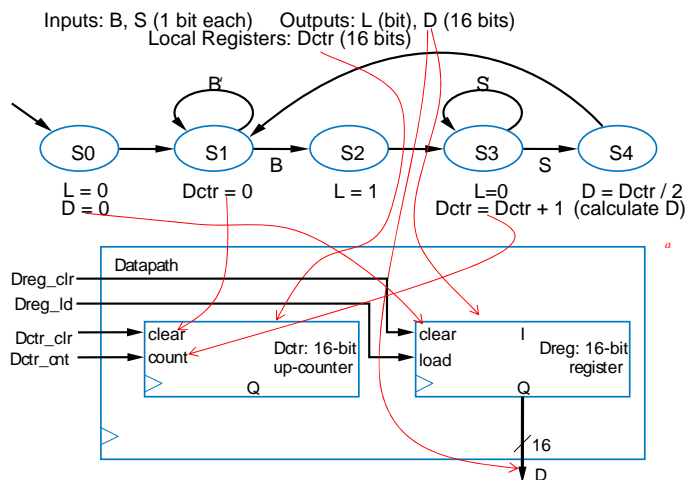- Make data inputs/outputs be datapath inputs/outputs
- Instantiate declared registers into the datapath (also instantiate a register for each data output)
- Examine every state and transition, and instantiate datapath components and connections to implement any data computations



Step 2 Example: Laser-Based Distance Measurer

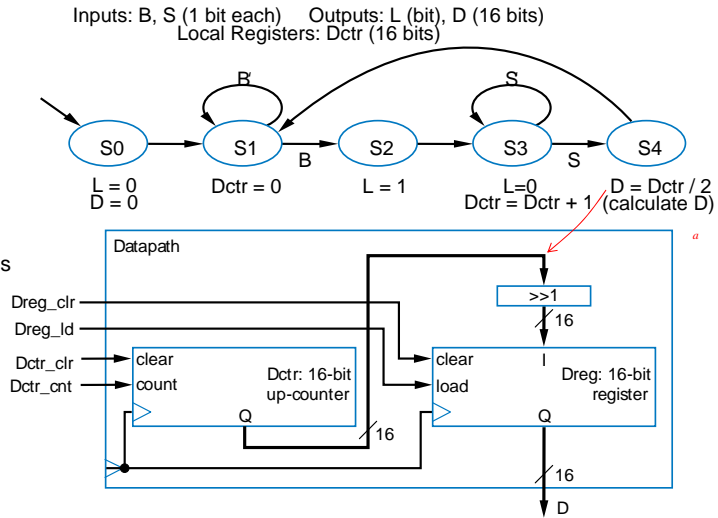(c) (continued)
Examine every state and transition, and instantiate datapath components and connections to implement any data computations




Digital Design
Copyright © 2006
Frank Vahid

21

Step 2 Example Showing Mux Use

Local registers
E, F, G, R (16 bits)

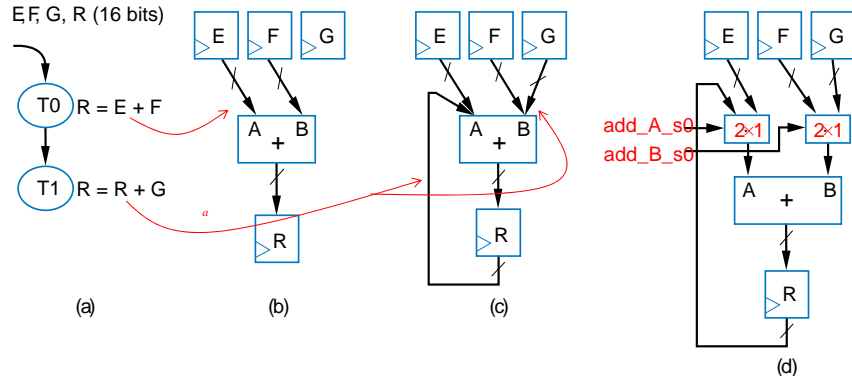


- Introduce mux when one component input can come from more than one source




Digital Design
Copyright © 2006
Frank Vahid

22

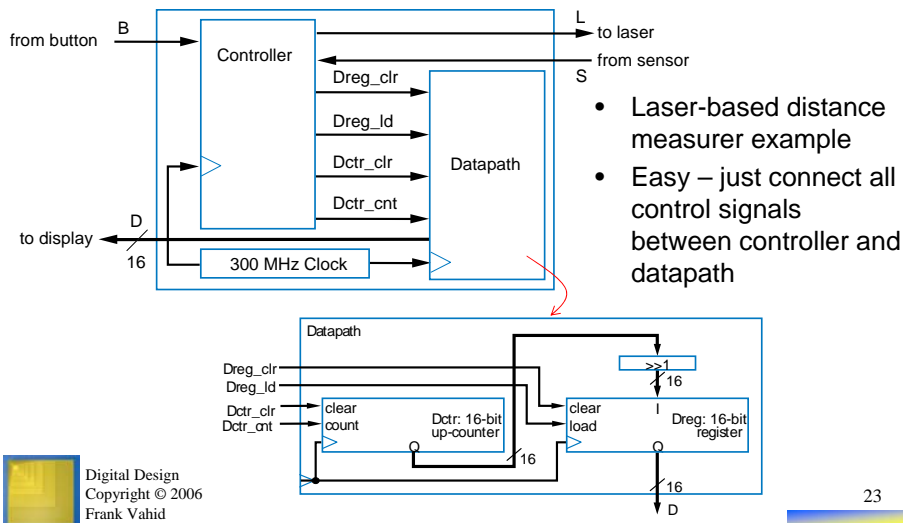
Step 3: Connecting the Datapath to a Controller




Step 4: Deriving the Controller's FSM

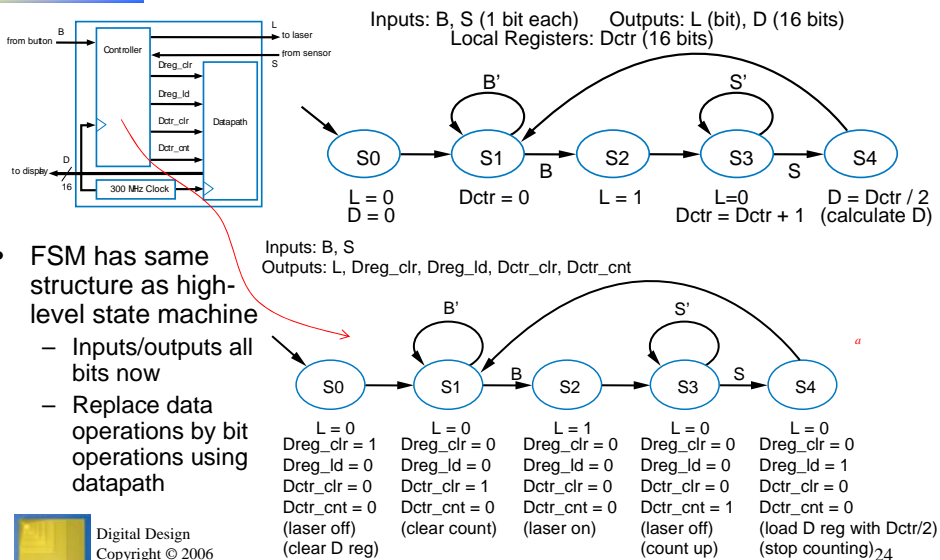

Step 4: Deriving the Controller's FSM

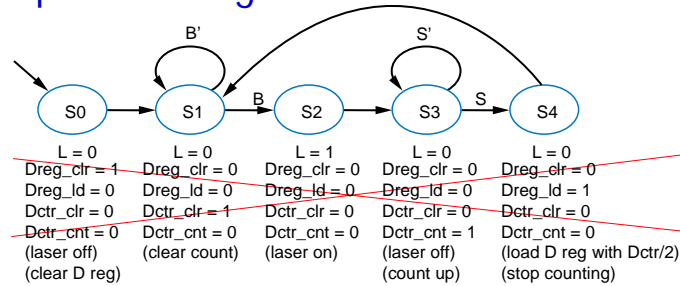

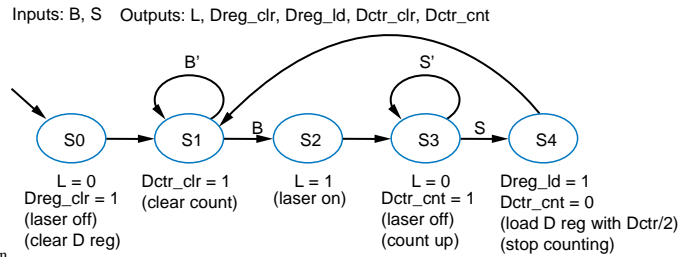
- Using shorthand of outputs not assigned implicitly assigned 0




Digital Design
Copyright © 2006
Frank Vahid

25

Step 4

 

 Inputs: B, S Outputs: L, Dreg_clr, Dreg_ld, Dctr_clr, Dctr_cnt



- Implement FSM as state register and logic (Ch3) to complete the design




Digital Design
Copyright © 2006
Frank Vahid

26

RTL Design Examples and Issues


- We'll use several more examples to illustrate RTL design
- Example: **Bus interface**
 - Master processor can read register from any peripheral
 - Each register has unique 4-bit address
 - Assume 1 register/periph.
 - Sets $rd=1$, $A=address$
 - Appropriate peripheral places register data on 32-bit D lines
 - Periph's address provided on $Faddr$ inputs (maybe from DIP switches, or another register)

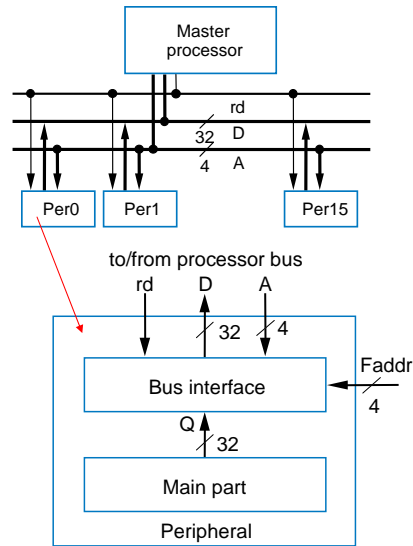

Digital Design
Copyright © 2006
Frank Vahid

27

RTL Example: Bus Interface

 



- Step 1: Create high-level state machine
 - State **WaitMyAddress**
 - Output “nothing” (“Z”) on D , store peripheral's register value Q into local register $Q1$
 - Wait until this peripheral's address is seen ($A=Faddr$) and $rd=1$
 - State **SendData**
 - Output $Q1$ onto D , wait for $rd=0$ (meaning main processor is done reading the D lines)



Digital Design
Copyright © 2006
Frank Vahid

28


RTL Example: Bus Interface

  

Digital Design
 Copyright © 2006
 Frank Vahid

29

RTL Example: Bus Interface

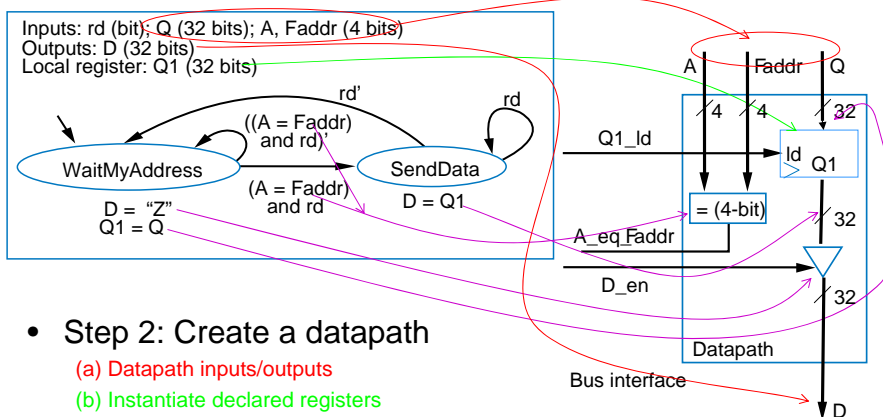

- Step 2: Create a datapath


- (a) Datapath inputs/outputs
- (b) Instantiate declared registers
- (c) Instantiate datapath components and connections



Digital Design
 Copyright © 2006
 Frank Vahid

30

RTL Example: Bus Interface

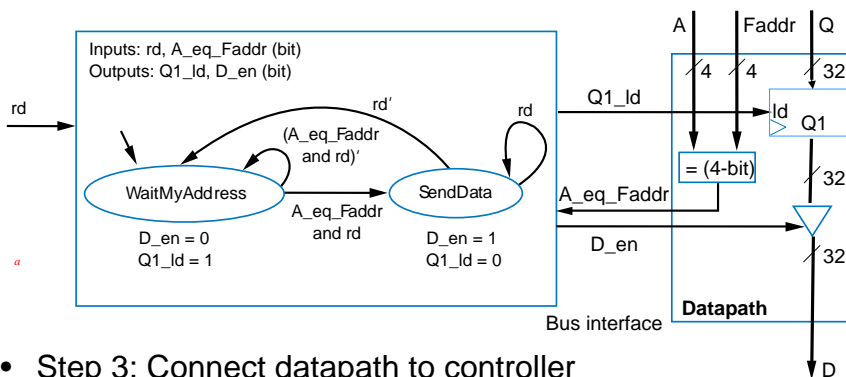


- Step 3: Connect datapath to controller
- Step 4: Derive controller's FSM



Digital Design
Copyright © 2006
Frank Vahid

31

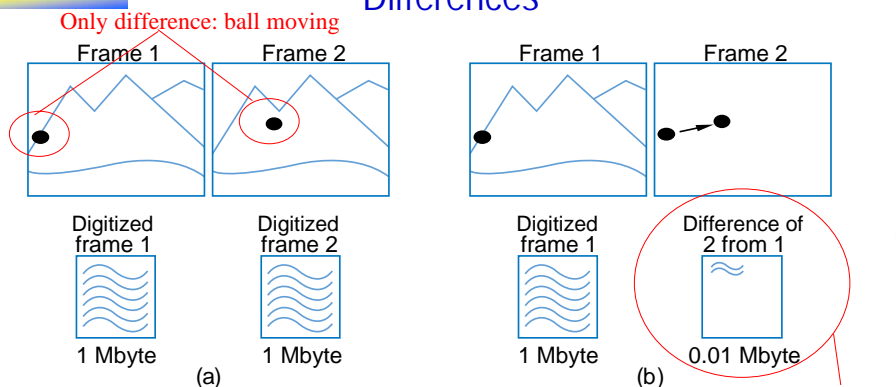RTL Example: Video Compression – Sum of Absolute Differences



- Video is a series of frames (e.g., 30 per second)
- Most frames similar to previous frame
 - Compression idea: just send difference from previous frame


Just send difference



Digital Design
Copyright © 2006
Frank Vahid

32

 RTL Example: Video Compression – Sum of Absolute Differences




- Need to quickly determine whether two frames are similar enough to just send difference for second frame
 - Compare corresponding 16x16 “blocks”
 - Treat 16x16 block as 256-byte array
 - Compute the absolute value of the difference of each array item
 - Sum those differences – if above a threshold, send complete frame for second frame; if below, can use difference method (using another technique, not described)



Digital Design
Copyright © 2006
Frank Vahid

33

 RTL Example: Video Compression – Sum of Absolute Differences




- Want fast sum-of-absolute-differences (SAD) component
 - When $go=1$, sums the differences of element pairs in arrays A and B , outputs that sum



Digital Design
Copyright © 2006
Frank Vahid


34

 RTL Example: Video Compression – Sum of Absolute Differences



Inputs: A, B (256 byte memory); go (bit)
 Outputs: sad (32 bits)
 Local registers: sum, sad_reg (32 bits); i (9 bits)

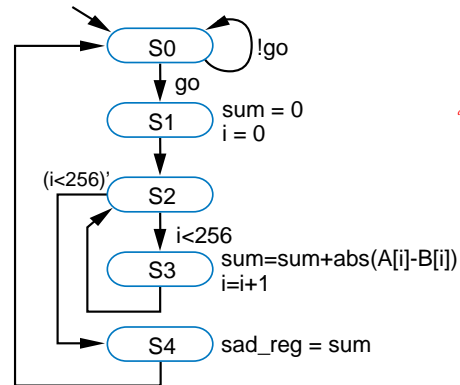- **S0**: wait for *go*
- **S1**: initialize *sum* and *index*
- **S2**: check if done ($i \geq 256$)
- **S3**: add difference to *sum*, increment index
- **S4**: done, write to output *sad_reg*





Digital Design
 Copyright © 2006
 Frank Vahid

35

RTL Example: Video Compression – Sum of Absolute Differences

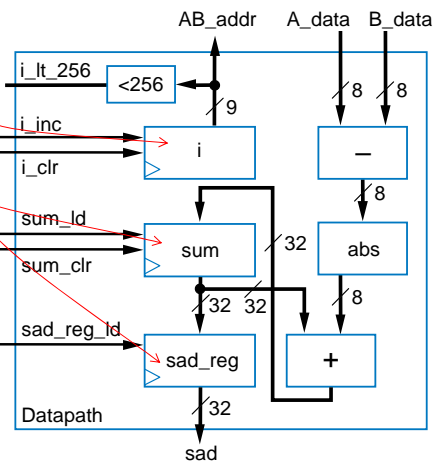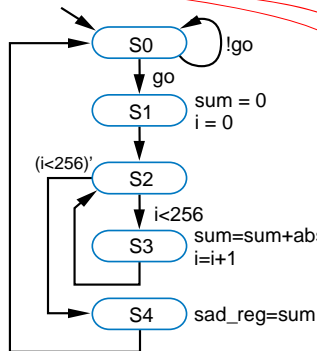Inputs: A, B (256 byte memory); go (bit)
 Outputs: sad (32 bits)
 Local registers: sum, sad_reg (32 bits); i (9 bits)




- **Step 2: Create datapath**



Digital Design
 Copyright © 2006
 Frank Vahid

36

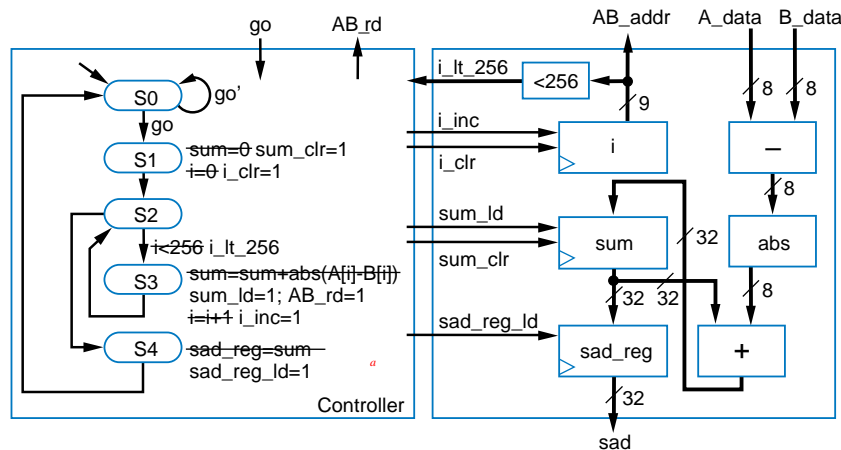RTL Example: Video Compression – Sum of Absolute Differences



- Step 3: Connect to controller
- Step 4: Replace high-level state machine by FSM




Digital Design
Copyright © 2006
Frank Vahid

37

RTL Example: Video Compression – Sum of Absolute Differences

- Comparing software and custom circuit SAD

- Circuit: Two states (**S2** & **S3**) for each i , 256 i s \rightarrow 512 clock cycles
- Software: Loop (for $i = 1$ to 256), but for each i , must move memory to local registers, subtract, compute absolute value, add to sum, increment i – say about 6 cycles per array item $\rightarrow 256 * 6 = 1536$ cycles
- Circuit is about 3 times (300%) faster
- Later, we'll see how to build SAD circuit that is even faster

 


Digital Design
Copyright © 2006
Frank Vahid

38

RTL Design Pitfalls and Good Practice

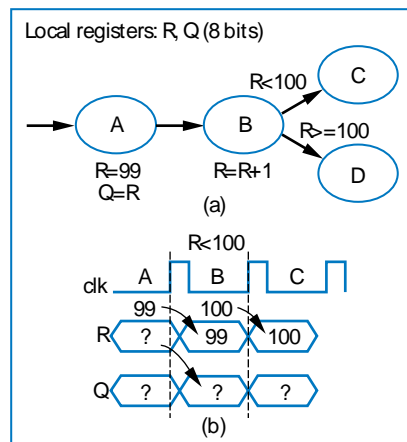- Common pitfall: Assuming register is update in the state it's written
 - Final value of Q ?
 - Final state?
 - Answers may surprise you
 - Value of Q unknown
 - Final state is **C**, not **D**
 - Why?
 - State **A**: $R=99$ and $Q=R$ happen simultaneously
 - State **B**: R not updated with $R+1$ until next clock cycle, simultaneously with state register being updated




Digital Design
Copyright © 2006
Frank Vahid

39

RTL Design Pitfalls and Good Practice

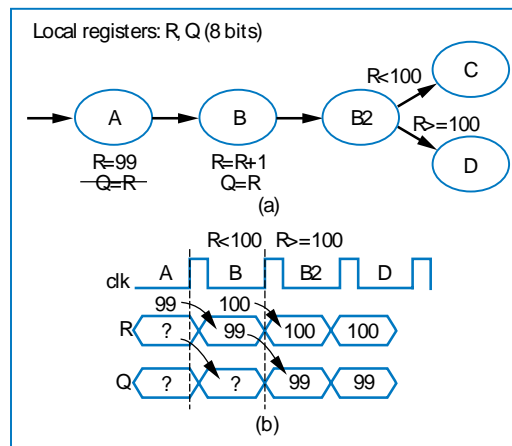- Solutions
 - Read register in following state ($Q=R$)
 - Insert extra state so that conditions use updated value
 - Other solutions are possible, depends on the example




Digital Design
Copyright © 2006
Frank Vahid

40

RTL Design Pitfalls and Good Practice

- Common pitfall: Reading outputs

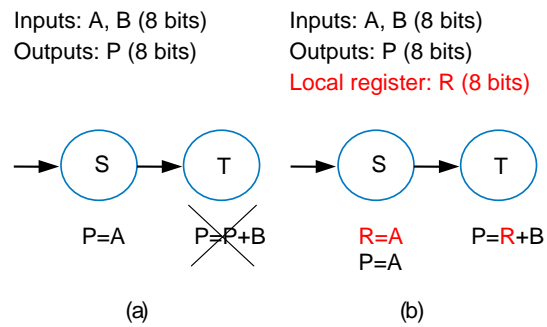
- Outputs can only be written
- Solution: Introduce additional register, which can be written and read



RTL Design Pitfalls and Good Practice

- Good practice: Register all data outputs

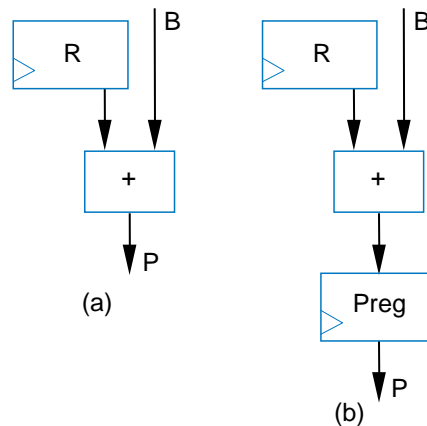- In fig (a), output P would show spurious values as addition computes
 - Furthermore, longest register-to-register path, which determines clock period, is not known until that output is connected to another component
- In fig (b), spurious outputs reduced, and longest register-to-register path is clear




Control vs. Data Dominated RTL Design

- Designs often categorized as control-dominated or data-dominated
 - Control-dominated design – Controller contains most of the complexity
 - Data-dominated design – Datapath contains most of the complexity
 - General, descriptive terms – no hard rule that separates the two types of designs
 - Laser-based distance measurer – control dominated
 - Bus interface, SAD circuit – mix of control and data
 - Now let's do a data dominated design



Data Dominated RTL Design Example: FIR Filter

 
- Filter concept
 - Suppose X is data from a temperature sensor, and particular input sequence is 180, 180, 181, 240, 180, 181 (one per clock cycle)
 - That 240 is probably wrong!
 - Could be electrical noise
 - Filter should remove such noise in its output Y
 - Simple filter: Output average of last N values
 - Small N : less filtering
 - Large N : more filtering, but less sharp output



Data Dominated RTL Design Example: FIR Filter

- FIR filter

- “Finite Impulse Response”
- Simply a configurable weighted sum of past input values
- $y(t) = c_0 \cdot x(t) + c_1 \cdot x(t-1) + c_2 \cdot x(t-2)$
 - Above known as “3 tap”
 - Tens of taps more common
 - Very general filter – User sets the constants (c_0 , c_1 , c_2) to define specific filter
- RTL design
 - Step 1: Create high-level state machine
 - But there really is none! Data dominated indeed.
 - Go straight to step 2

 

Digital Design
Copyright © 2006
Frank Vahid

45

Data Dominated RTL Design Example: FIR Filter


- Step 2: Create datapath

- Begin by creating chain of x_t registers to hold past values of X



$$y(t) = c_0 \cdot x(t) + c_1 \cdot x(t-1) + c_2 \cdot x(t-2)$$

Suppose sequence is: 180, 181, 240

 

Digital Design
Copyright © 2006
Frank Vahid

46


Data Dominated RTL Design Example: FIR Filter

- Step 2: Create datapath (cont.)

- Instantiate registers for c_0, c_1, c_2
- Instantiate multipliers to compute $c*x$ values


 
$$y(t) = c_0 * x(t) + c_1 * x(t-1) + c_2 * x(t-2)$$



Digital Design
Copyright © 2006
Frank Vahid

47


Data Dominated RTL Design Example: FIR Filter

- Step 2: Create datapath (cont.)

- Instantiate adders


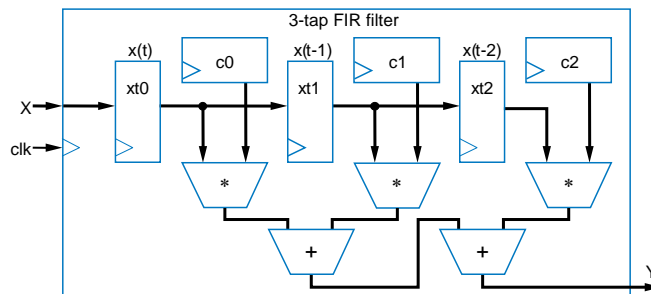
$$y(t) = c_0 * x(t) + c_1 * x(t-1) + c_2 * x(t-2)$$



Digital Design
Copyright © 2006
Frank Vahid

48


Data Dominated RTL Design Example: FIR Filter

- Step 2: Create datapath (cont.)

- Add circuitry to allow loading of particular c register


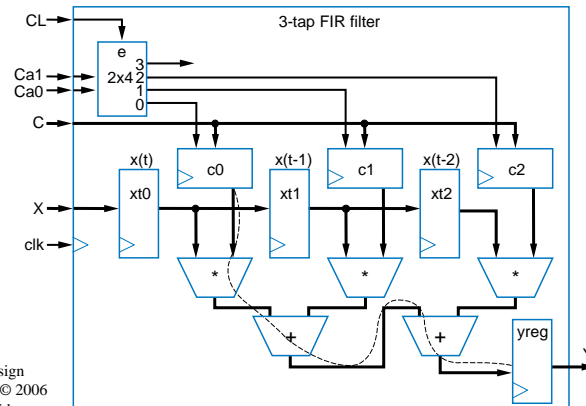
$$y(t) = c_0 * x(t) + c_1 * x(t-1) + c_2 * x(t-2)$$



Digital Design
Copyright © 2006
Frank Vahid

49

Data Dominated RTL Design Example: FIR Filter

- Step 3 & 4: Connect to controller, Create FSM

- No controller needed
- Extreme data-dominated example
- (Example of an extreme control-dominated design – an FSM, with no datapath)

- Comparing the FIR circuit to a software implementation

- Circuit
 - Assume adder has 2-gate delay, multiplier has 20-gate delay
 - Longest path goes through one multiplier and two adders
 - $20 + 2 + 2 = 24$ -gate delay
 - 100-tap filter, following design on previous slide, would have about a 34-gate delay: 1 multiplier and 7 adders on longest path
- Software
 - 100-tap filter: 100 multiplications, 100 additions. Say 2 instructions per multiplication, 2 per addition. Say 10-gate delay per instruction.
 - $(100 * 2 + 100 * 2) * 10 = 4000$ gate delays
- Circuit is more than 100 times faster (10,000% faster). Wow.




Digital Design
Copyright © 2006
Frank Vahid

50


Determining Clock Frequency

 - Designers of digital circuits often want fastest performance
 - Means want high clock frequency
- Frequency limited by **longest register-to-register delay**
 - Known as **critical path**
 - If clock is any faster, incorrect data may be stored into register
 - Longest path on right is 2 ns
 - Ignoring wire delays, and register setup and hold times, for simplicity




Critical Path

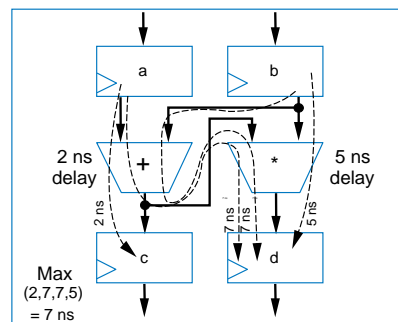- Example shows four paths
 - a to c through +: 2 ns
 - a to d through + and *: 7 ns
 - b to d through + and *: 7 ns
 - b to d through *: 5 ns
- Longest path is thus 7 ns
- Fastest frequency
 - $1 / 7 \text{ ns} = 142 \text{ MHz}$



Critical Path Considering Wire Delays

- Real wires have delay too
 - Must include in critical path
- Example shows two paths
 - Each is $0.5 + 2 + 0.5 = 3$ ns
- Trend
 - 1980s/1990s: Wire delays were tiny compared to logic delays
 - But wire delays not shrinking as fast as logic delays
 - Wire delays may even be greater than logic delays!
- Must also consider register setup and hold times, also add to path
- Then add some time to the computed path, just to be safe
 - e.g., if path is 3 ns, say 4 ns instead

 


Digital Design
Copyright © 2006
Frank Vahid

53

A Circuit May Have Numerous Paths

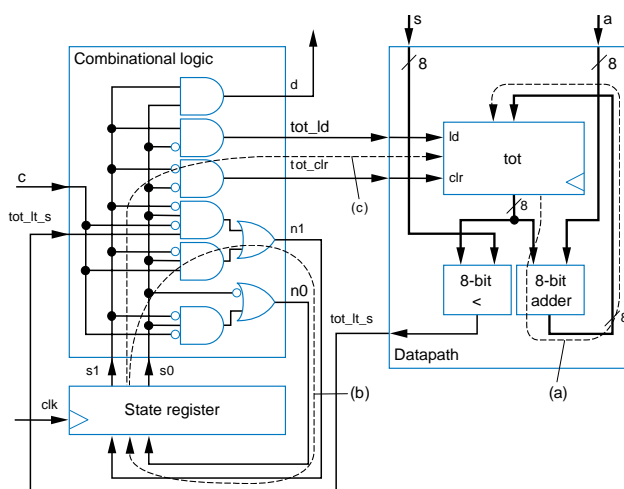
- Paths can exist
 - In the datapath
 - In the controller
 - Between the controller and datapath
 - May be hundreds or thousands of paths
- Timing analysis tools that evaluate all possible paths automatically very helpful



Digital Design
Copyright © 2006
Frank Vahid

54

Behavioral Level Design: C to Gates

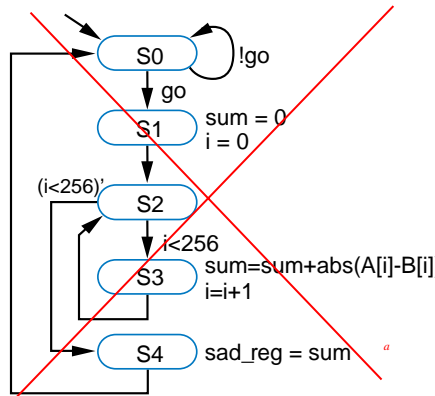

C code

```
int SAD (byte A[256], byte B[256]) // not quite C syntax
{
    uint sum; short uint i;
    sum = 0;
    i = 0;
    while (i < 256) {
        sum = sum + abs(A[i] - B[i]);
        i = i + 1;
    }
    return sum;
}
```

- Earlier sum-of-absolute-differences example
 - Started with high-level state machine
 - C code is an even better starting point -- easier to understand



Digital Design
Copyright © 2006
Frank Vahid

55

Behavioral-Level Design: Start with C (or Similar Language)

- Replace first step of RTL design method by two steps
 - Capture in C, then convert C to high-level state machine
 - How convert from C to high-level state machine?

Step 1A: Capture in C

Step 1B: Convert to high-level state machine

Step	Description
Step 1	Capture a high-level state machine. Describe the system's desired behavior as a high-level state machine. The state machine consists of states and transitions. The state machine is "high-level" because the transition conditions and the state actions are more than just Boolean operations on bit inputs and outputs.
Step 2	Create a datapath. Create a datapath to carry out the data operations of the high-level state machine.
Step 3	Connect the datapath to a controller. Connect the datapath to a controller block. Connect external Boolean inputs and outputs to the controller block.
Step 4	Derive the controller's FSM. Convert the high-level state machine to a finite-state machine (FSM) for the controller, by replacing data operations with setting and reading of control signals to and from the datapath.




Digital Design
Copyright © 2006
Frank Vahid

56

Converting from C to High-Level State Machine

 - Convert each C construct to equivalent states and transitions
- *Assignment* statement
 - Becomes one state with assignment
- *If-then* statement
 - Becomes state with condition check, transitioning to “then” statements if condition true, otherwise to ending state
 - “then” statements would also be converted to states




Digital Design
Copyright © 2006
Frank Vahid

57

Converting from C to High-Level State Machine

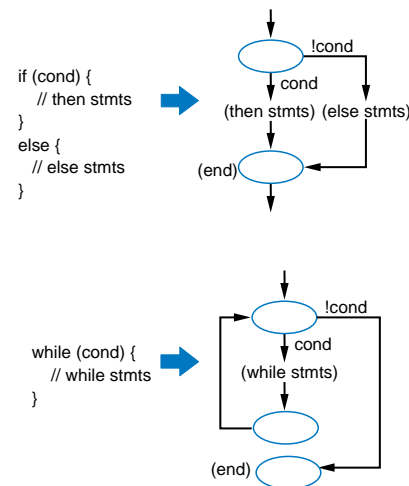- *If-then-else*
 - Becomes state with condition check, transitioning to “then” statements if condition true, or to “else” statements if condition false
- *While loop* statement
 - Becomes state with condition check, transitioning to while loop’s statements if true, then transitioning back to condition check




Digital Design
Copyright © 2006
Frank Vahid

58

Simple Example of Converting from C to High-Level State Machine

Inputs: uint X, Y
Outputs: uint Max
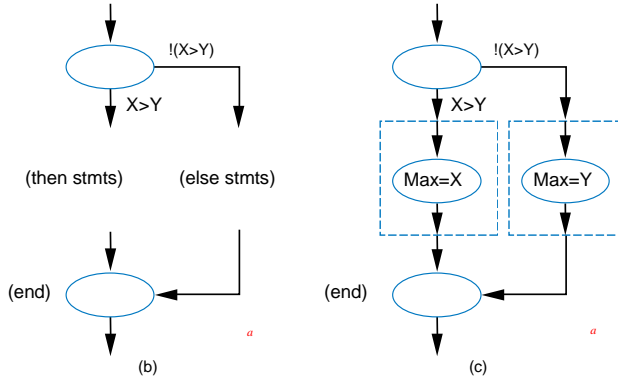
```
if (X > Y) {
    Max = X;
}
else {
    Max = Y;
}
```



- Simple example: Computing the maximum of two numbers
 - Convert if-then-else statement to states (b)
 - Then convert assignment statements to states (c)




Digital Design
Copyright © 2006
Frank Vahid

59

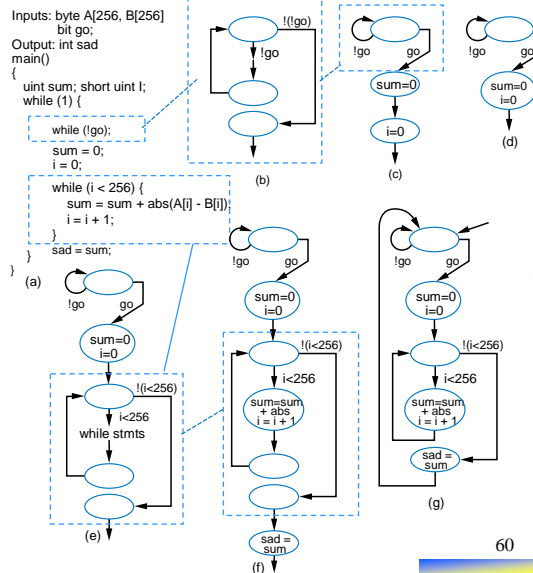Example: Converting Sum-of-Absolute-Differences C code to High-Level State Machine

- Convert each construct to states
 - Simplify when possible, e.g., merge states
- From high-level state machine, follow RTL design method to create circuit
- Thus, can convert C to gates using straightforward automatable process
 - Not all C constructs can be efficiently converted
 - Use C subset if intended for circuit
 - Can use languages other than C, of course




Digital Design
Copyright © 2006
Frank Vahid

60

Memory Components

 - Register-transfer level design instantiates datapath components to create datapath, controlled by a controller
 - A few more components are often used outside the controller and datapath
- ***MxN memory***
 - M words, N bits wide each
- Several varieties of memory, which we now introduce





Digital Design
Copyright © 2006
Frank Vahid

61

Random Access Memory (RAM)


- RAM – Readable and writable memory
 - “Random access memory”
 - Strange name – Created several decades ago to contrast with sequentially-accessed storage like tape drives
 - Logically same as register file – Memory with address inputs, data inputs/outputs, and control
 - RAM usually just one port; register file usually two or more
 - RAM vs. register file
 - RAM typically larger than *roughly* 512 or 1024 words
 - RAM typically stores bits using a bit storage approach that is more efficient than a flip flop
 - RAM typically implemented on a chip in a square rather than rectangular shape – keeps longest wires (hence delay) short

  

Digital Design
Copyright © 2006
Frank Vahid

62

RAM Internal Structure

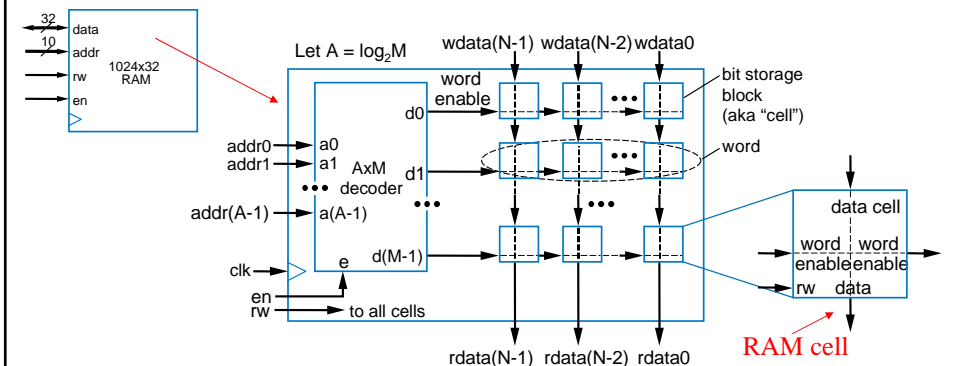


- Similar internal structure as register file
 - Decoder enables appropriate word based on address inputs
 - rw controls whether cell is written or read
 - Let's see what's inside each RAM cell





Digital Design
Copyright © 2006
Frank Vahid

63

Static RAM (SRAM)

 

  - "Static" RAM cell
 - 6 transistors (recall inverter is 2 transistors)
 - Writing this cell
 - word enable input comes from decoder
 - When 0, value d loops around inverters
 - That loop is where a bit stays stored
 - When 1, the data bit value enters the loop
 - data is the bit to be stored in this cell
 - data' enters on other side
 - Example shows a "1" being written into cell



Digital Design
Copyright © 2006
Frank Vahid

64

Static RAM (SRAM)

Let $A = \log_2 M$

1024x32 RAM

- “Static” RAM cell
 - Reading this cell
 - Somewhat trickier
 - When rw set to read, the RAM logic sets both $data$ and $data'$ to 1
 - The stored bit d will pull either the left line or the right bit down slightly below 1
 - “Sense amplifiers” detect which side is slightly pulled down
 - The electrical description of SRAM is really beyond our scope – just general idea here, mainly to contrast with DRAM...

Digital Design
Copyright © 2006
Frank Vahid

65

Dynamic RAM (DRAM)

1024x32 RAM


- “Dynamic” RAM cell
 - 1 transistor (rather than 6)
 - Relies on *large* capacitor to store bit
 - Write: Transistor conducts, data voltage level gets stored on top plate of capacitor
 - Read: Just look at value of d
 - Problem: Capacitor discharges over time
 - Must “refresh” regularly, by reading d and then writing it right back

Digital Design
Copyright © 2006
Frank Vahid

66

Comparing Memory Types

 - Register file
 - Fastest
 - But biggest size
- SRAM
 - Fast
 - More compact than register file
- DRAM
 - Slowest
 - And refreshing takes time
 - But very compact
- Use register file for small items, SRAM for large items, and DRAM for huge items
 - Note: DRAM's big capacitor requires a special chip design process, so DRAM is often a separate chip





Size comparison for same number of bits (not to scale)



Digital Design
Copyright © 2006
Frank Vahid

67

Reading and Writing a RAM

  


- Writing
 - Put address on *addr* lines, data on *data* lines, set $rw=1$, $en=1$
- Reading
 - Set *addr* and *en* lines, but put nothing (Z) on *data* lines, set $rw=0$
 - Data will appear on *data* lines
- Don't forget to obey setup and hold times
 - In short – keep inputs stable before and after a clock edge



Digital Design
Copyright © 2006
Frank Vahid

68

RAM Example: Digital Sound Recorder

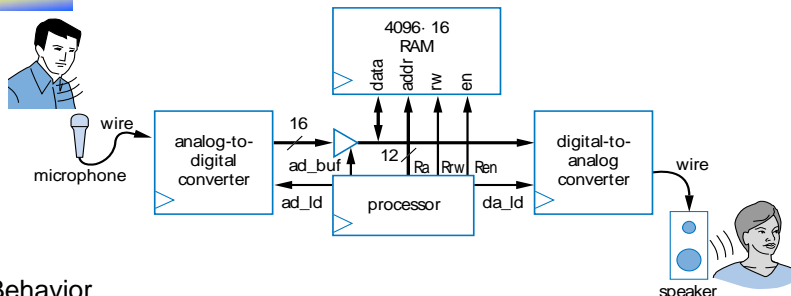

- Behavior
 - Record: Digitize sound, store as series of 4096 12-bit digital values in RAM
 - We'll use a 4096x16 RAM (12-bit wide RAM not common)
 - Play back later
 - Common behavior in telephone answering machine, toys, voice recorders
- To record, processor should read a-to-d, store read values into successive RAM words
 - To play, processor should read successive RAM words and enable d-to-a




Digital Design
Copyright © 2006
Frank Vahid

69

RAM Example: Digital Sound Recorder

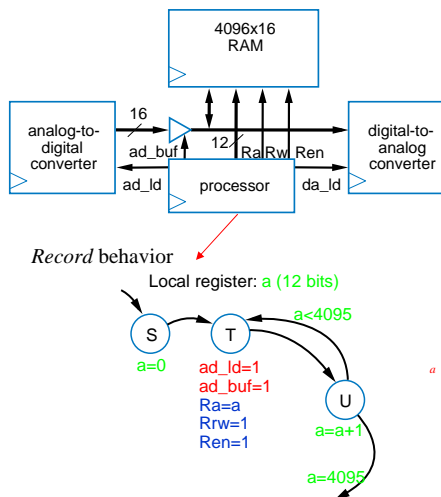- RTL design of processor
 - Create high-level state machine
 - Begin with the *record* behavior
 - Keep local register *a*
 - Stores current address, ranges from 0 to 4095 (thus need 12 bits)
 - Create state machine that counts from 0 to 4095 using *a*
 - For each *a*
 - Read analog-to-digital conv.
 - » $ad_ld=1, ad_buf=1$
 - Write to RAM at address *a*
 - » $Ra=a, Rrw=1, Ren=1$




Digital Design
Copyright © 2006
Frank Vahid

70

RAM Example: Digital Sound Recorder

- Now create *play* behavior
- Use local register *a* again, create state machine that counts from 0 to 4095 again
 - For each *a*
 - Read RAM
 - Write to digital-to-analog conv.
 - Note: Must write d-to-a one cycle *after* reading RAM, when the read data is available on the data bus
- The record and play state machines would be parts of a larger state machine controlled by signals that determine when to record or play

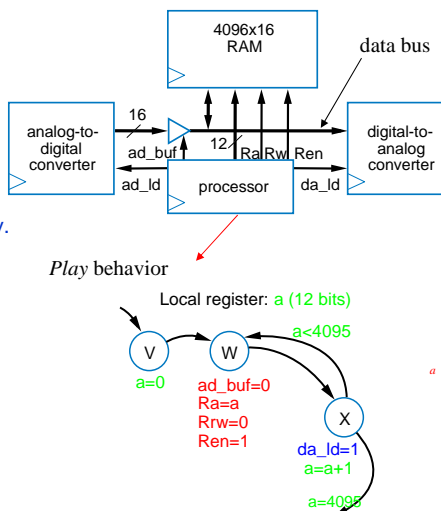


Digital Design
Copyright © 2006
Frank Vahid


71

Read-Only Memory – ROM

- Memory that can only be read from, not written to
 - Data lines are output only
 - No need for *rw* input
- Advantages over RAM
 - Compact: May be smaller
 - **Nonvolatile**: Saves bits even if power supply is turned off
 - Speed: May be faster (especially than DRAM)
 - Low power: Doesn't need power supply to save bits, so can extend battery life
- Choose ROM over RAM if stored data won't change (or won't change often)
 - For example, a table of Celsius to Fahrenheit conversions in a digital thermometer

 

RAM block symbol

 


ROM block symbol



Digital Design
Copyright © 2006
Frank Vahid


72

Read-Only Memory – ROM

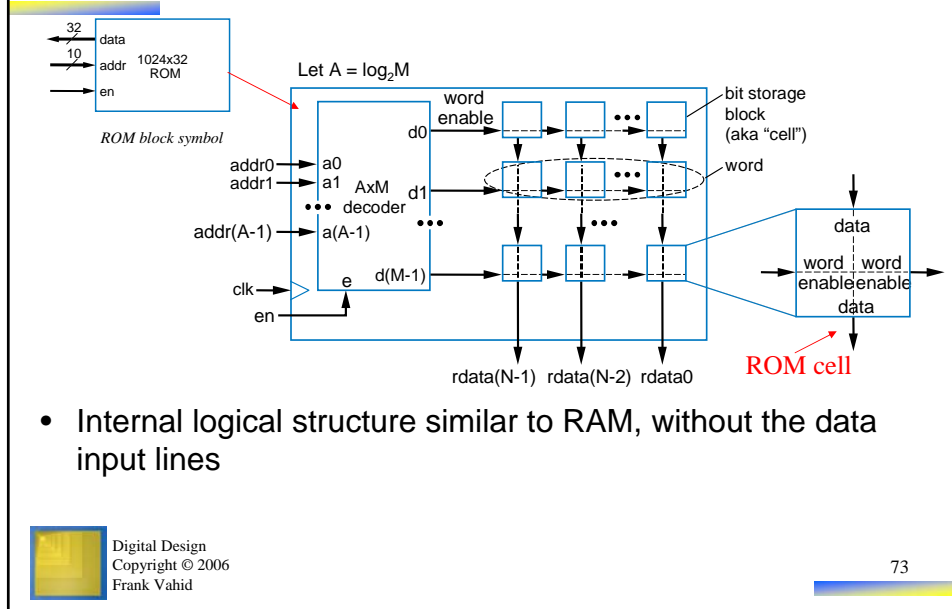

ROM Types


- If a ROM can only be read, how are the stored bits stored in the first place?
 - Storing bits in a ROM known as *programming*
 - Several methods
- Mask-programmed ROM**
 - Bits are hardwired as 0s or 1s during chip manufacturing
 - 2-bit word on right stores "10"
 - word enable (from decoder) simply passes the hardwired value through transistor
 - Notice how compact, and fast, this memory would be

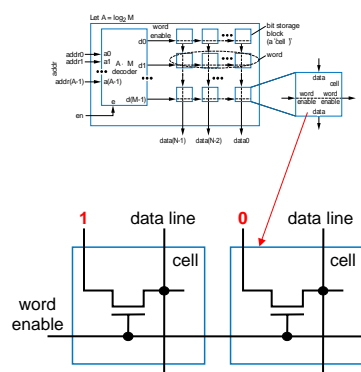

ROM Types

- **Fuse-Based Programmable ROM**

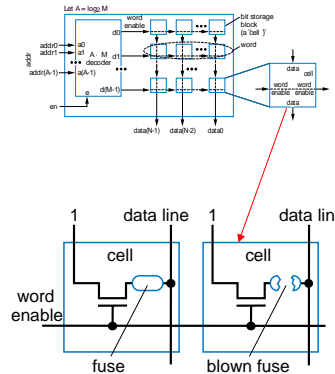- Each cell has a fuse
- A special device, known as a programmer, blows certain fuses (using higher-than-normal voltage)
 - Those cells will be read as 0s (involving some special electronics)
 - Cells with unblown fuses will be read as 1s
 - 2-bit word on right stores “10”
- Also known as **One-Time Programmable (OTP) ROM**





Digital Design
Copyright © 2006
Frank Vahid

75

ROM Types

- **Erasable Programmable ROM (EPROM)**

- Uses “floating-gate transistor” in each cell
- Special programmer device uses higher-than-normal voltage to cause electrons to *tunnel* into the gate
 - Electrons become trapped in the gate
 - Only done for cells that should store 0
 - Other cells (without electrons trapped in gate) will be 1
 - 2-bit word on right stores “10”
 - Details beyond our scope – just general idea is necessary here
- To erase, shine ultraviolet light onto chip
 - Gives trapped electrons energy to escape
 - Requires chip package to have window

 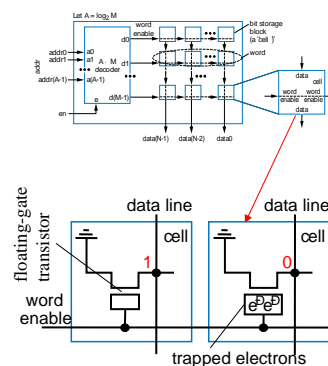


Digital Design
Copyright © 2006
Frank Vahid

76

ROM Types


- **Electrically-Erasable Programmable ROM (EEPROM)**
 - Similar to EPROM
 - Uses floating-gate transistor, electronic programming to trap electrons in certain cells
 - But erasing done *electronically*, not using UV light
 - Erasing done one word at a time
- **Flash memory**
 - Like EEPROM, but all words (or large blocks of words) can be erased *simultaneously*
 - Become common relatively recently (late 1990s)
- Both types are in-system programmable
 - Can be programmed with new stored bits while in the system in which the ROM operates
 - Requires bi-directional data lines, and write control input
 - Also need busy output to indicate that erasing is in progress – erasing takes some time

 

Digital Design
Copyright © 2006
Frank Vahid

77

ROM Example: Talking Doll

 


- Doll plays prerecorded message, trigger by vibration
 - Message must be stored without power supply → Use a ROM, not a RAM, because ROM is nonvolatile
 - And because message will never change, use a mask-programmed ROM or OTP ROM
 - Processor should wait for vibration ($v=1$), then read words 0 to 4095 from the ROM, writing each to the d-to-a



Digital Design
Copyright © 2006
Frank Vahid

78

ROM Example: Talking Doll

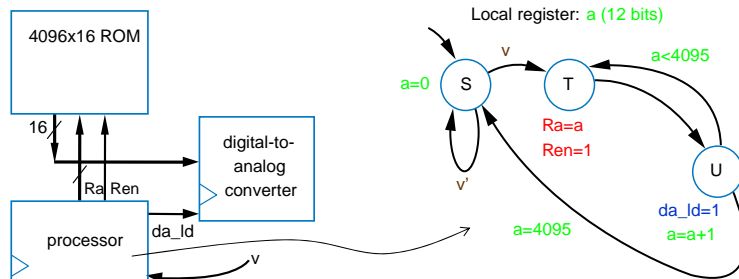

- High-level state machine
 - Create state machine that waits for $v=1$, and then counts from 0 to 4095 using a local register a
 - For each a , read ROM, write to digital-to-analog converter




Digital Design
Copyright © 2006
Frank Vahid

79

ROM Example: Digital Telephone Answering Machine Using a Flash Memory

- Want to record the outgoing announcement
 - When $rec=1$, record digitized sound in locations 0 to 4095
 - When $play=1$, play those stored sounds to digital-to-analog converter
- What type of memory?
 - Should store without power supply – ROM, not RAM
 - Should be in-system programmable – EEPROM or Flash, not EPROM, OTP ROM, or mask-programmed ROM
 - Will always erase entire memory when reprogramming – Flash better than EEPROM

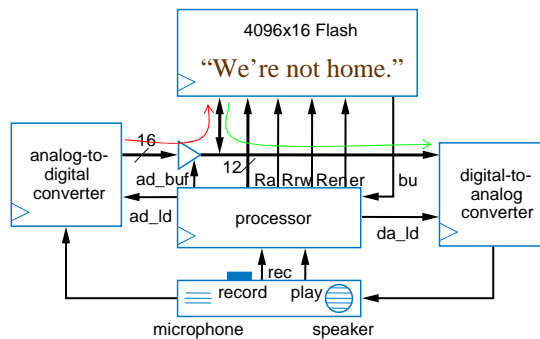


Digital Design
Copyright © 2006
Frank Vahid

80

ROM Example: Digital Telephone Answering Machine Using a Flash Memory

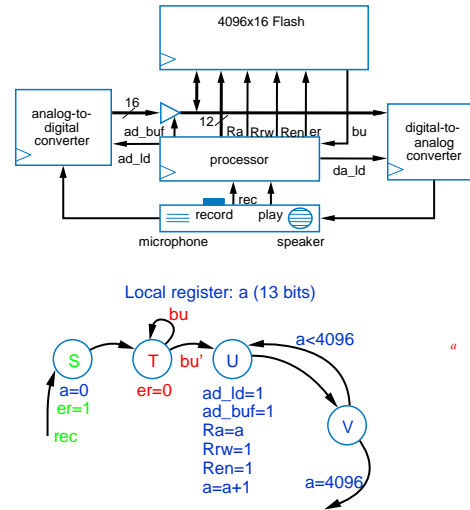- High-level state machine
 - Once $rec=1$, begin erasing flash by setting $er=1$
 - Wait for flash to finish erasing by waiting for $bu=0$
 - Execute loop that sets local register a from 0 to 4095, reading analog-to-digital converter and writing to flash for each a




Digital Design
Copyright © 2006
Frank Vahid

81

Blurring of Distinction Between ROM and RAM

- We said that
 - RAM is readable and writable
 - ROM is read-only
- But some ROMs act almost like RAMs
 - EEPROM and Flash are in-system programmable
 - Essentially means that writes are slow
 - Also, number of writes may be limited (perhaps a few million times)
- And, some RAMs act almost like ROMs
 - Non-volatile RAMs: Can save their data without the power supply
 - One type: Built-in battery, may work for up to 10 years
 - Another type: Includes ROM backup for RAM – controller writes RAM contents to ROM before turning off
- New memory technologies evolving that merge RAM and ROM benefits
 - e.g., MRAM
- Bottom line
 - Lot of choices available to designer, must find best fit with design goals

 


Digital Design
Copyright © 2006
Frank Vahid

82


Queues

 - A queue is another component sometimes used during RTL design
- **Queue**: A list written to at the back, from read from the front
 - Like a list of waiting restaurant customers
- Writing called a **push**, reading called a **pop**
- Because first item written into a queue will be the first item read out, also called a **FIFO** (first-in-first-out)




Queues

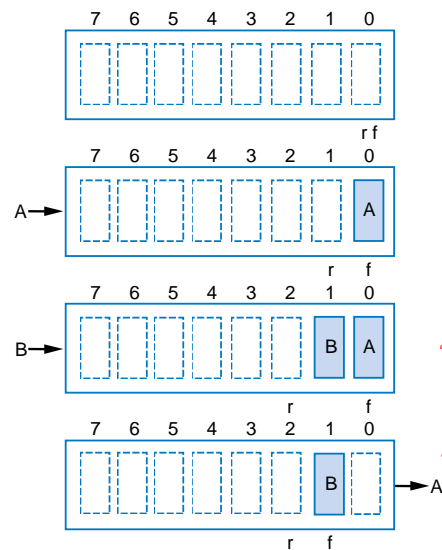- Queue has addresses, and two pointers: *rear* and *front*
 - Initially both point to 0
- Push (write)
 - Item written to address pointed to by *rear*
 - *rear* incremented
- Pop (read)
 - Item read from address pointed to by *front*
 - *front* incremented
- If front or rear reaches 7, next (incremented) value should be 0 (for a queue with addresses 0 to 7)



Queues

- Treat memory as a circle
 - If front or rear reaches 7, next (incremented) value should be 0 rather than 8 (for a queue with addresses 0 to 7)
- Two conditions of interest
 - Full queue – no room for more items
 - In 8-entry queue, means 8 items present
 - No further pushes allowed until a pop occurs
 - Causes front=rear
 - Empty queue – no items
 - No pops allowed until a push occurs
 - Causes front=rear
 - Both conditions have front=rear
 - To detect whether front=rear means full or empty, need state machine that detects if previous operation was push or pop, sets full or empty output signal (respectively)

 


Digital Design
Copyright © 2006
Frank Vahid

85

Queue Implementation

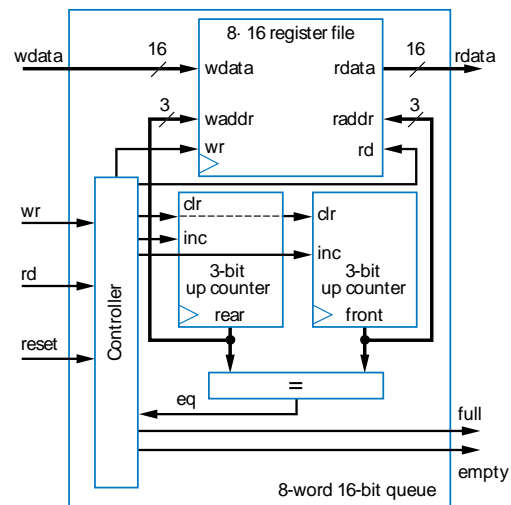- Can use register file for item storage
- Implement *rear* and *front* using up counters
 - rear used as register file's write address, front as read address
- Simple controller would set control lines for pushes and pops, and also detect full and empty situations
 - FSM for controller not shown



Digital Design
Copyright © 2006
Frank Vahid

86

Common Uses of a Queue

- Computer keyboard
 - Pushes pressed keys onto queue, meanwhile pops and sends to computer
- Digital video recorder
 - Pushes captured frames, meanwhile pops frames, compresses them, and stores them
- Computer network routers
 - Pushes incoming packets onto queue, meanwhile pops packets, processes destination information, and forwards each packet out over appropriate port




Digital Design
Copyright © 2006
Frank Vahid

87

Queue Usage Example

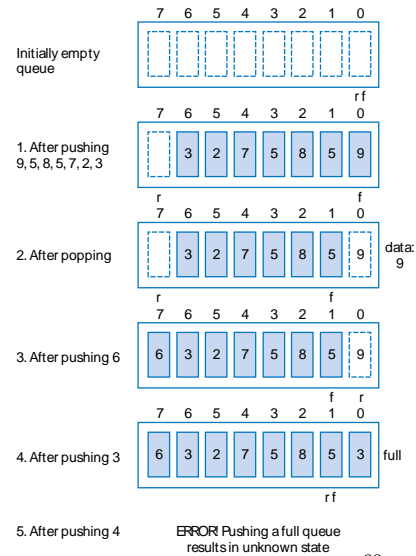- Example series of pushes and pops
 - Note how rear and front pointers move
 - Note that popping doesn't really remove the data from the queue, but that data is no longer accessible
 - Note how rear (and front) wraps around from address 7 to 0
- Note: pushing a full queue is an error
 - As is popping an empty queue




Digital Design
Copyright © 2006
Frank Vahid


88

Hierarchy – A Key Design Concept

- Hierarchy
 - An organization with a few items at the top, with each item decomposed into other items
 - Common example: A country
 - 1 item at the top (the country)
 - Country item decomposed into state/province items
 - Each state/province item decomposed into city items
- Hierarchy helps us **manage complexity**
 - To go from transistors to gates, muxes, decoders, registers, ALUs, controllers, datapaths, memories, queues, etc.
 - Imagine trying to comprehend a controller and datapath at the level of gates

 

Map showing all levels of hierarchy

 


Map showing just top two levels of hierarchy





Hierarchy and Abstraction

 - Abstraction
 - Hierarchy often involves not just grouping items into a new item, but also associating higher-level behavior with the new item, known as **abstraction**
 - e.g., an 8-bit adder has an understandable high-level behavior – it adds two 8-bit binary numbers
 - Frees designer from having to remember, or even from having to understand, the lower-level details



Hierarchy and Composing Larger Components from Smaller Versions

- A common task is to compose smaller components into a larger one
 - Gates: Suppose you have plenty of 3-input AND gates, but need a 9-input AND gate
 - Can simple compose the 9-input gate from several 3-input gates
 - Muxes: Suppose you have 4x1 and 2x1 muxes, but need an 8x1 mux
 - s2 selects either top or bottom 4x1
 - s1s0 select particular 4x1 input
 - Implements 8x1 mux – 8 data inputs, 3 selects, one output

  


Digital Design
Copyright © 2006
Frank Vahid

91

Hierarchy and Composing Larger Components from Smaller Versions

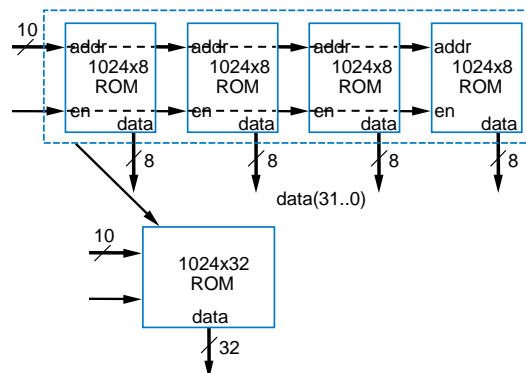- Composing memory very common
- Making memory words wider
 - Easy – just place memories side-by-side until desired width obtained
 - Share address/control lines, concatenate data lines
 - Example: Compose 1024x8 ROMs into 1024x32 ROM





Digital Design
Copyright © 2006
Frank Vahid

92

Hierarchy and Composing Larger Components from Smaller Versions

 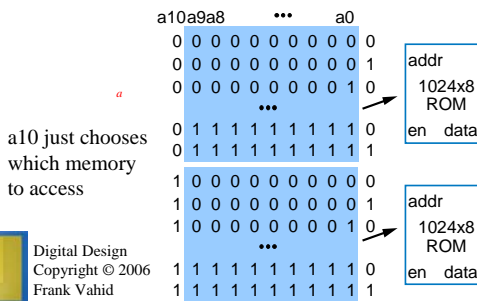- Creating memory with more words
 - Put memories on top of one another until the number of desired words is achieved
 - Use decoder to select among the memories
 - Can use highest order address input(s) as decoder input
 - Although actually, any address line could be used
 - Example: Compose 1024x8 memories into 2048x8 memory



To create memory with more words and wider words, can first compose to enough words, then widen.

Digital Design
Copyright © 2006
Frank Vahid

Chapter Summary

- Modern digital design involves creating processor-level components
- Four-step RTL method can be used
 - 1. High-level state machine 2. Create datapath 3. Connect datapath to controller 4. Derive controller FSM
- Several example
 - Control dominated, data dominated, and mix
- Determining fastest clock frequency
 - By finding critical path
- Behavioral-level design – C to gates
 - By using method to convert C (subset) to high-level state machine
- Additional RTL components
 - Memory: RAM, ROM
 - Queues
- Hierarchy: A key concept used throughout Chapters 2-5

Digital Design
Copyright © 2006
Frank Vahid